

# Introduction to Behavioural VHDL

---

**Virendra Singh**

Professor

Dept. of Electrical Engineering, and  
Dept. of Computer Science & Engg.  
Indian Institute of Technology Bombay

<http://www.ee.iitb.ac.in/~viren/>

E-mail: [viren@{ee,cse}.iitb.ac.in](mailto:viren@{ee,cse}.iitb.ac.in)



7<sup>th</sup> June 2024



# VLSI Realization Process

---

**Customer's need**

**Determine requirements**

**Write specifications**

**Design synthesis and Verification**

**Test development**


**Fabrication**

**Manufacturing test**

**Chips to customer**


 
# The Role of Hardware Description Languages



- Design is structured around a hierarchy of representations
- HDLs can describe distinct aspects of a design at multiple levels of abstraction

# Basic VHDL Concepts

---

- Interfaces
- Modeling (Behavior, Dataflow, Structure)
- Test Benches
- Analysis, elaboration, simulation
- Synthesis



# Behavioral VHDL



07 Jun 2024

viren@IITB-NPTEL

5



# Assignment Statement

---

- Signal assignment
- Variable assignment

**Signal** STAT\_OUT: Std\_Logic;

Stat\_out <= **not** state\_in;

**Variable** Preset, count:unsigned (0 to 3);

Count := preset +1;

# Logical Operators

---

Library IEEE;

Use IEEE.Std\_logic\_1164.all;

Entity Full\_Adder is

Port (A, B, CIN: in Std\_logic;

sum, cout: out Std\_logic);

Architecture Dataflow of Full\_adder is

Begin

sum <= (A xor B) xor CIN;

Cout <= (A and B) or (B and CIN) or (A and CIN);

End;



# Arithmetic Operators

---

Library IEEE;

Use IEEE.numeric\_std.all;

Entity Unsigned\_Adder is

Port (A, B: in unsigned (0 to 3);

sum: out unsigned (0 to 3));

Architecture Simple of Unsigned\_adder is

Begin

sum <= A + B;

End Simple;





# Relational Operators

---

library IEEE;

use IEEE.numeric\_std.all;

entity GT is

port (A, B: in unsigned (3 downto 0);

    Z: out Boolean);

architecture DF of GT is

begin

    Z <= A (1 down to 0) > B (3 downto 2);

end Simple;



# Vector and Slices

---

Library IEEE;

Use IEEE.std\_logic\_1164.all;

package ARRAYS is

Type BANK is array (0 to 1) of Std\_logic\_vector (3 downto 0);

End ARRAYS;

Library IEEE;

Use IEEE.std\_logic\_1164.all , work.arrays.all;

entity GT is

port (A, B, C: in std\_logic\_vector (3 downto 0);

REG\_FILE: inout BANK;

Z: out std\_logic\_vector (3 downto 0));

end GT;



# Inferring Latches from If Statements

---

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.numeric_std.all;  
  
entity INCR is  
port (A: in bit;  
      Z: out unsigned (0 to 1));  
End INCR;
```



# Inferring Latches from If Statements

---

architecture Example of INCR is

Begin

INCR\_L: process (A)

variable ONES: unsigned (0 to 1)

begin

if A = '1' then

ONES := ONES + 1;

end if;

Z <= ONES;

end process INCR\_L;

end Example;



# Inferring Latches from If Statements

Package EXAM is

    type GRADE\_TYPE is (FAIL, PASS, EXCELLENT);

end;

library IEEE;

use IEEE.std\_logic\_1164.all;

use work.exam.all;

Entity compute is

port (marks: in natural in range 0 to 10;

    grade: out GRADE\_TYPE);

End compute;



# Inferring Latches from If Statements

---

architecture Example of compute is

begin

    process (marks)

    begin

        if marks < 5 then

            grade <= FAIL;

        elsif marks >= 5 and marks < 7 then

            grade <= PASS;

        end if;

    end process ;

end Example;



# Inferring Latches from If Statements

---

Package EXAM is

    type GRADE\_TYPE is (FAIL, PASS, EXCELLENT);

end;

library IEEE;

use IEEE.std\_logic\_1164.all;

use work.exam.all;

Entity compute\_mod is

port (marks: in natural in range 0 to 10;

    grade: out GRADE\_TYPE);

End compute\_mod;



# Inferring Latches from If Statements

---

architecture Example of compute\_mod is

begin

    process (marks)

    begin

        if marks < 5 then

            grade <= FAIL;

        elsif marks >= 5 and marks < 7 then

            grade <= PASS;

        else grade <= EXCELLENT;

        end if;

    end process ;

end Example;





# Inferring Latches from If Statements: Exception for Variables

---

signal A, B, clk;

....

P1: process (A, clk)

    variable p: std\_logic;

begin

    if clk = '1' then

        B <= p;

        p := A;

    end if;

end process ;



# Inferring Latches from If Statements: Exception for Variables

---

```
P2: process (A, clk)
    variable q: std_logic;
begin
    if clk = '1' then
        q := A;
        B <= q;
    end if;
end process P2;
end
```



# Case Statements

---

Package PACK\_A is

    type OP\_TYPE is (ADD, SUB, MUL, DIV);

end;

library IEEE;

use IEEE.std\_logic\_1164.all, IEEE.numeric\_std.all;

use work.exam.all;

Entity ALU is

port (OP: in OP\_TYPE;

        A, B: in unsigned (0 to 1);

        Z: out unsigned (0 to 1));

End ALU;

# Case Statements

---

architecture Example of ALU is

begin

    process (OP, A, B)

        variable tmp: unsigned (3 downto 0);

    begin

        case OP is

            when ADD =>

                Z <= A + B;

            when SUB =>

                Z <= A - B;



# Case Statements

---

when MUL =>

tmp := A \* B;

Z <= tmp (1 downto 0);

when DIV =>

Z <= A / B;

end case;

end process ;

end Example;



# Case Statements

---

```
package COLLECT is
    type STATES is (S0, S1, S2, S3);
end;
library IEEE;
use IEEE.std_logic_1164.all, work.pack_b.all;
entity state_update is
    port (curr_state: in STATES;
          Z: out integer range 0 to 3);
end state_update;
```



# Case Statements

---

architecture Example of state\_update is

begin

    process (curr\_state)

        variable tmp: unsigned (3 downto 0);

    begin

        case curr\_state is

            when S0 | S3 =>

                Z <= 0;

            when S1 =>

                Z <= 3;

            when others =>

                null;

        end case;

    end process;

end Example;



# Case Statements

architecture Example of state\_update is

begin

    process (curr\_state)

        variable tmp: unsigned (3 downto 0);

    begin

        Z <= 0;

        case curr\_state is

            when S0 | S3 =>

                Z <= 0;

            when S1 =>

                Z <= 3;

            when others =>

                null;

        end case;

    end process;

End Example;





# FSM Implementation

---

```
architecture fsm_1 of fsm is
    signal cur_state: fsm_state;
    signal nxt_state: fsm_state;

    State_change: process(clk, reset)
    begin
        if (clk'event and clk=1)
            if reset = '1' then
                cur_state <= S0;
            else
                cur_state <= nxt_state;
            end if;
        end if;
    end process state_change;
```



# FSM Implementation

```
Next_state_logic: process(cur_state, reset)
begin
  case cur_state is
    when S0 =>
      if ready = '1' then
        nxt_state <= S1;
      else
        nxt_state <= S0;
      end if;
    when S1 =>
      nxt_state <= S2;
      . . . . .
  end case;
end process;
```



# FSM Implementation

```
Output_logic: process(cur_state)
begin
  case cur_state is
    when S0 =>
      A <= '0';
      B <= '0';
      C <= '00";
      D <= "00";
    when S1 =>
      A <= '1';
      B <= '0';
      C <= '11";
      D <= "01";
    ....
  end case
end process;
end;
```



# Loop Statements

---

3 kinds of loop in VHDL

- While-loop
- For – loop
- Loop

For-loop is supported by synthesis



# Loop Statements

---

```
library IEEE;  
use IEEE.std_logic_1164.all, IEEE.numeric_std.all;  
entity DEMUX is  
  port (A: in unsigned (1 downto 0);  
        Z: out unsigned (3 downto 0));  
end DEMUX;
```



# Loop Statements

```
architecture For_Loop of DEMUX is
begin
    process (A)
        variable tmp: integer range 0 to 3;
    begin
        tmp := to_integer (A);
        for J in Z`range loop
            if tmp = J then
                Z(J) <= '1';
            end if;
        end loop;
    end process ;
end Example;
```



# Wait Statements

---

3 kinds of loop in VHDL

- Wait for *time*
- Wait until *condition*
- Wait on *signal-list*

**Wait until** is supported by synthesis

Implies synchronous logical behaviour

If used, it should be the first statement in the process

Condition must be one of the allowed clock expressions

- **Wait until** *clock-name = clock\_value;*
- **Wait until** *clock-name = clock\_value and clock\_name`EVENT;*



# Loop Statements

```
library IEEE;  
use IEEE.std_logic_1164.all, IEEE.numeric_std.all;  
Entity INCR is  
port (clk: in std_logic;  
      counter: out unsigned (1 downto 0));  
end DEMUX;  
architecture FLOP of INCR is  
Begin  
    process  
    begin  
        wait until clk = '1';  
        counter <= counter + 1;  
    end process;  
End FLOP;
```





# Loop Statements

```
architecture For_Loop of DEMUX is
begin
    process (A)
        variable tmp: integer range 0 to 3;
    begin
        tmp := To_integer (A);
        for J in Z`range loop
            if tmp = J then
                Z(J) <= '1';
            end if;
        end loop;
    end process ;
end Example;
```



# Modeling Memories

---

- RAM can be modeled as registers
- Storage represented by array, bit vectors, or integers
- An address vector, converted to integer, is used to index the array
- Declaration of an array type and a signal of that type

```
type mem_array is array (0 to 2**depth -1) of  
    std_ulogic_vector(width -1 downto 0);  
signal RAM: mem_array;
```

# Asynchronous RAM

---

- Level sensitive device
- Model like a latch
- Behaviour model

```
Asynch_RAM: process (addr, din, we)
begin
    if we = '1' then
        RAM(to_integer (addr)) <= din;
    end if;
end process ;
dout <= RAM (to_integer (addr));
```

# Synchronous RAM with Asynchronous Read

- Write operation is synchronous
- Have embedded registers that store address and data
- Read is asynchronous

Synch\_RAM: `process` (clk)

`begin`

`if rising_edge (clk) then`

`if we = '1' then`

`RAM(to_integer (addr)) <= din ;`

`end if;`

`end if;`

`end process ;`

`dout <= RAM (to_integer (addr));`

# Synchronous RAM with Synchronous Read

- Have embedded registers that store address and data
- Differ in data they read when write is also performed

```
Synch_RAM:  process (clk)
begin
    if rising_edge (clk) then
        dout <= RAM (to_integer (addr));
        if we = '1' then
            RAM(to_integer (addr)) <= din ;
        end if;
    end if;
end process Synch_RAM;
```



# Synchronous RAM with Synchronous Read

- Have embedded registers that store address and data
- Differ in data they read when write is also performed

```
Synch_RAM:  process (clk)
begin
    if rising_edge (clk) then
        if we = '1' then
            RAM(to_integer (addr)) <= din ;
        end if;
        dout <= RAM (to_integer (addr));
    end if;
end process Synch_RAM;
```



# Synchronous RAM with Synchronous Read

- Have embedded registers that store address and data
- Differ in data they read when write is also performed
- Provides new data

Synch\_RAM: `process` (clk)

`begin`

`if rising_edge (clk) then`

`if we = '1' then`

`RAM(to_integer (addr)) <= din ;`

`else`

`dout <= RAM (to_integer (addr));`

`end if;`

`end if;`

`end process` Synch\_RAM;



# Synchronous RAM with Synchronous Read

- Add enable input

Synch\_RAM:   process (clk)

begin

    if rising\_edge (clk) then

        if en = '1' then

            dout <= RAM (to\_integer (addr));

        if we = '1' then

            RAM(to\_integer (addr)) <= din ;

        end if;

    end if;

end if;

end process Synch\_RAM;





# Thanks

